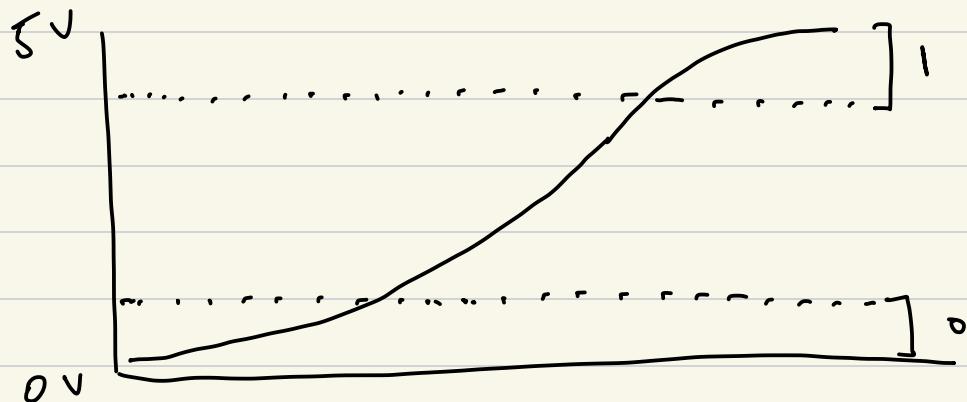


CS315-01 Lab Intro to Digital Design

Digital Design

Analog \rightarrow Digital



wires \nsubseteq devices \rightarrow gates

AND



OR



NOT



$$\text{C code} \quad r = a \& b$$

$$r = a \wedge b$$

$$r = a \cdot a$$

$$\text{Boolean algebra} \quad r = a \cdot b$$

$$r = a + b$$

$$r = \bar{a}$$

$$\text{Logic} \quad r = a \wedge b$$


$$r = a \vee b$$

$$r = \neg a$$

a	b	r
0	0	0
0	1	0
1	0	0
1	1	1

a	b	r
0	0	0
0	1	1
1	0	1
1	1	1


a	r
0	1
1	0

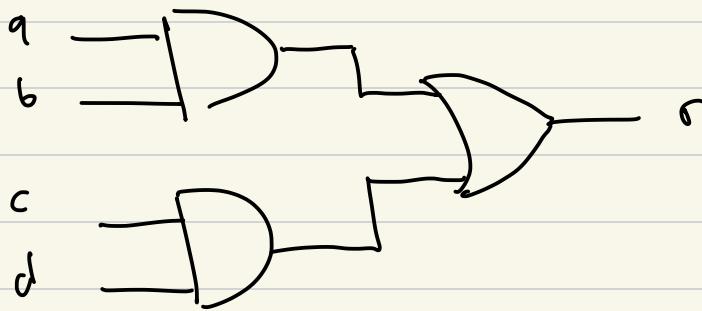

$$r = (a \cdot b) + (c \cdot d)$$

Abstraction in Digital Logic

Goal: build an 8-bit adder

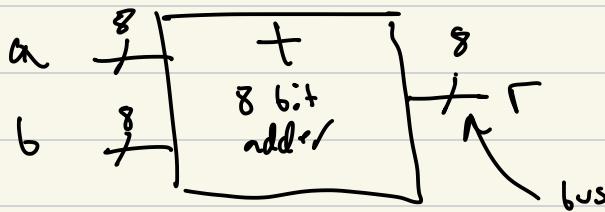

Sum - of - products

Sum of two 1-bit numbers

a	b	sum
0	0	0
0	1	1
1	0	1
1	1	0

XOR


$$\text{sum} = a \oplus b$$




$$\text{sum} = (\bar{a} \cdot b) + (a \cdot \bar{b})$$

$$a = 0 \quad b = 1$$
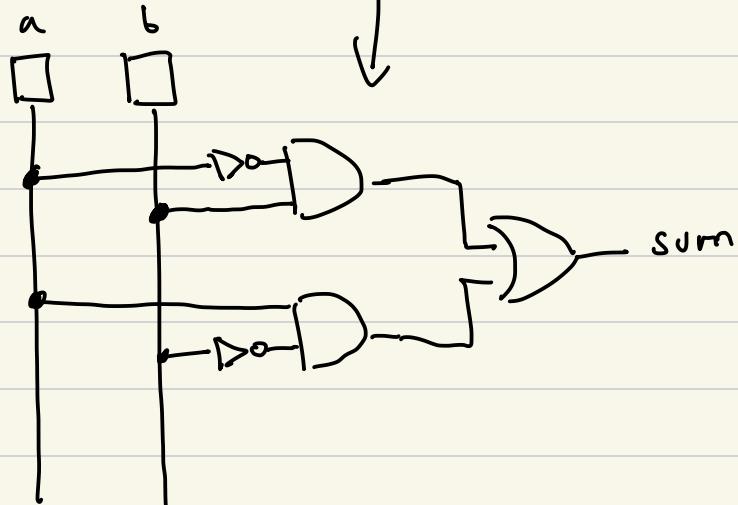
$$\begin{aligned}\text{sum} &= (\bar{0} \cdot 1) + (0 \cdot \bar{1}) \\ &= (1 \cdot 1) + (0 \cdot 0) \\ &= 1 + 0 \\ &= 1\end{aligned}$$



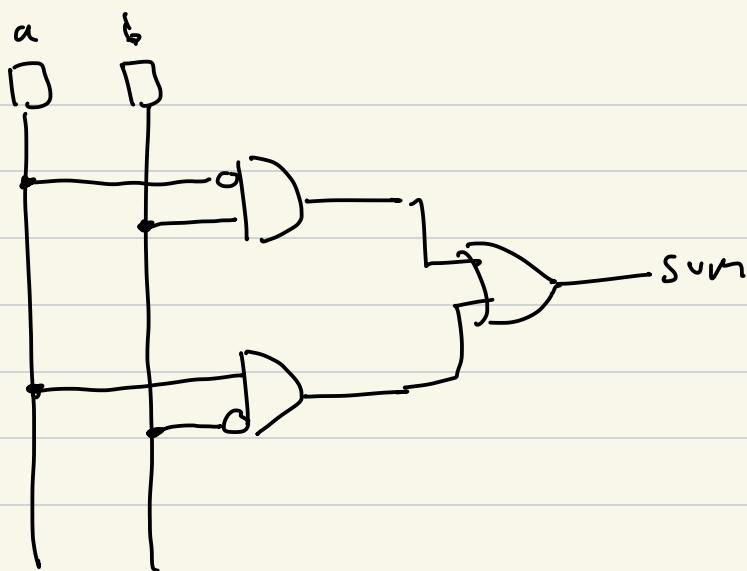

sum-of-products

1) Build a truth table for your function

For Each output

2) Identify rows with output of 1

3) Construct product (\cdot) terms for each row

- a) If input is 1 \rightarrow do not invert input var
- b) If input is 0 \rightarrow invert input var

4) Sum (+) all product terms