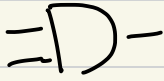


CS 315-01 Combinational Logic Address

AND




OR




NOT



Sum-of-products

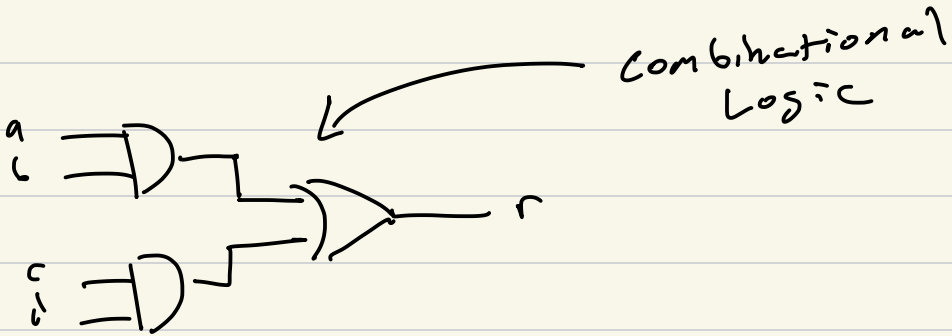

Goal:

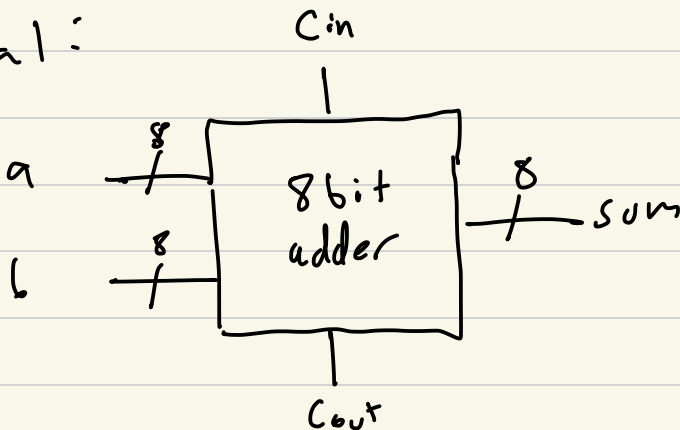

Sum-of-products

A new function

3-bit number $n_2 n_1 n_0$ (bits)

Two 1-bit outputs: even odd

Goal: determine if the number of "1" bits is even or odd

1 1 0 even
1 1 1 odd
1 0 0 odd


Sum-of-products

- 1) truth table
- 2) Look at rows with output of 1
- 3) form SOP equation

n_2	n_1	n_0	even	<u>odd</u>
0	0	0	1	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	0	1

$$\text{even} = (\bar{n}_2 \cdot \bar{n}_1 \cdot \bar{n}_0) + (\bar{n}_2 \cdot n_1 \cdot n_0) + (n_2 \cdot \bar{n}_1 \cdot n_0) + (n_2 \cdot n_1 \cdot \bar{n}_0)$$

$$\text{odd} = \overline{\text{even}}$$

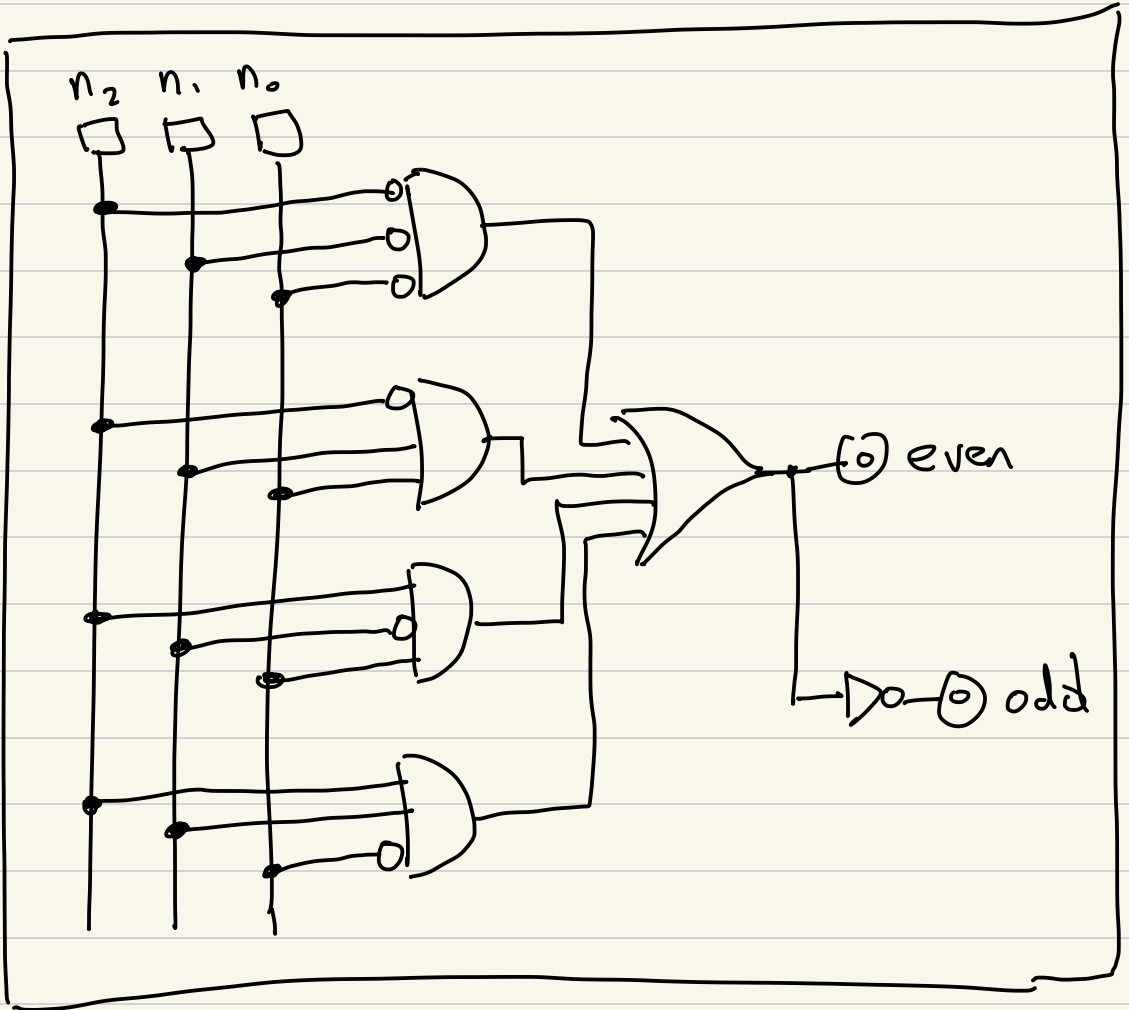

Disited Components

even-odd-bits

even-odd-multi

Lab 04 Part 2 Max 2

$\sqrt[2\text{bits}]{a_1 a_0}$ $\sqrt[2\text{bits}]{b_1 b_0}$ $\sqrt[2\text{bits}]{r_1 r_0}$


$a_1 a_0$	$b_1 b_0$	$r_1 r_0$
⋮	⋮	⋮
⋮	⋮	⋮
1 0	0 1	1 0
⋮	⋮	⋮
⋮	⋮	⋮
⋮	⋮	⋮
⋮	⋮	⋮

$r_1 =$ _____


$r_0 =$ _____

hint:
use not
invert
to reduce the
number of
product term

1 bit Adder

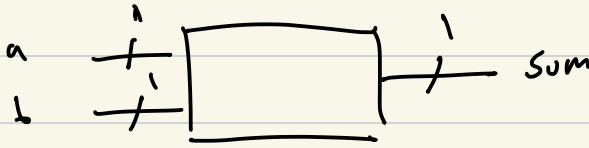


1 bit
half adder

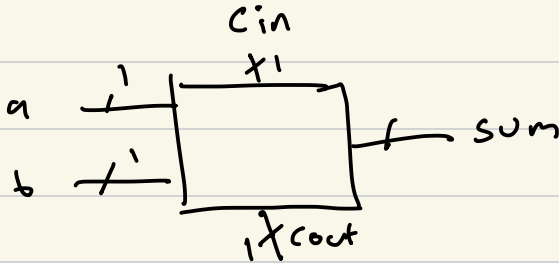


1 bit
full adder


Build truth table (Part 3)

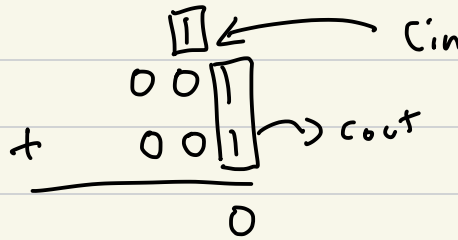

1 bit full adder component


layout mode

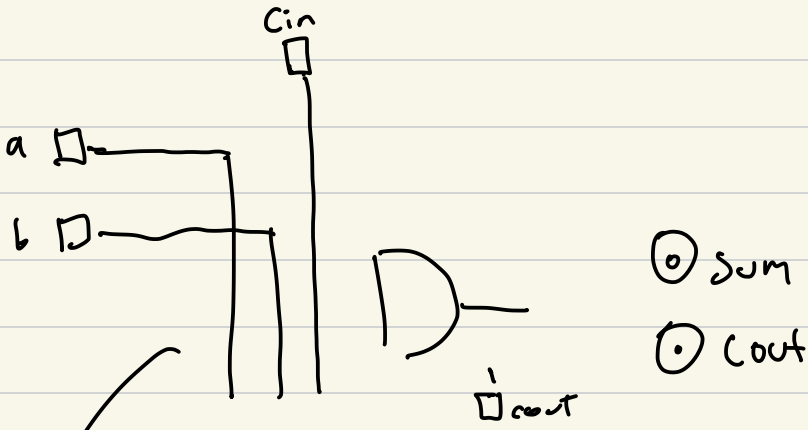

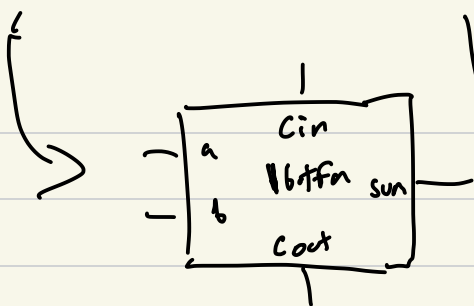


could
 $a_7 a_6 a_5 a_4 a_3 a_2 a_1 a_0 b_7 b_6 b_5 \dots$
 17 inputs
 $2^{17} =$

8 bit ripple-carry adder

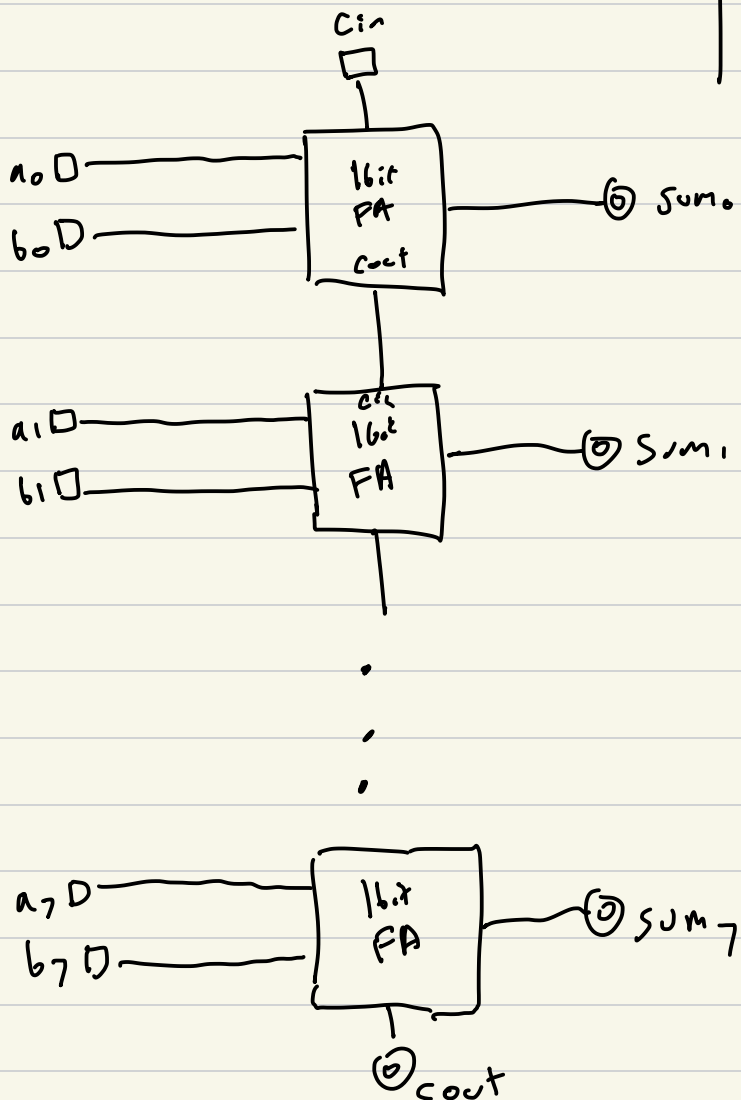

FA = Full Adder

8 data bits


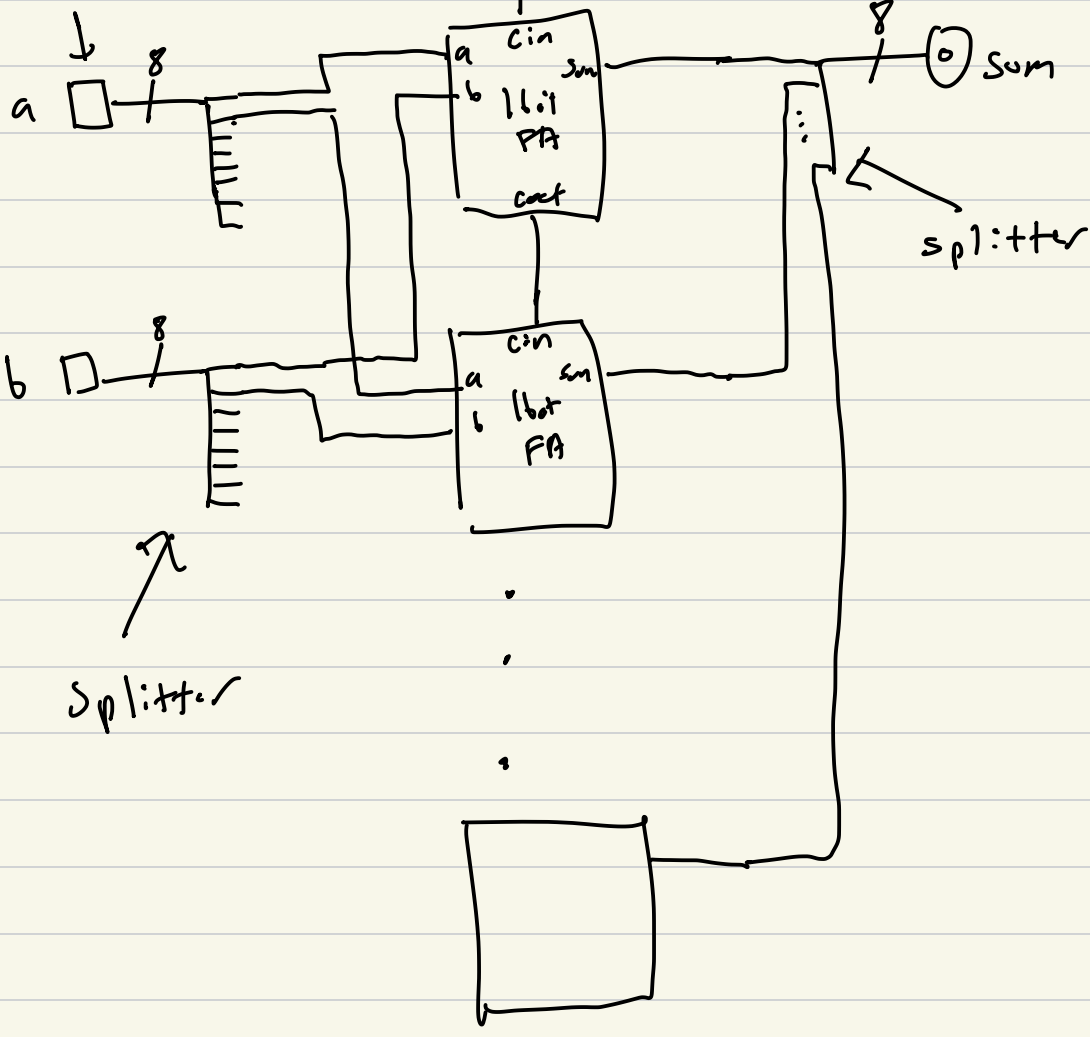


Subtraction


$$A - B = A + (-B) \quad \text{for 2's comp}$$

↑ invert
and add 1

← constant
1

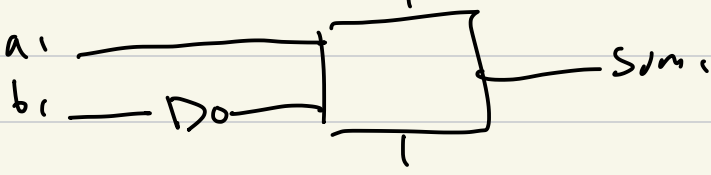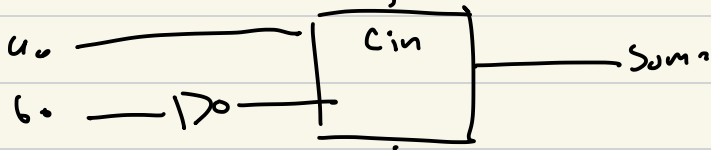


⋮

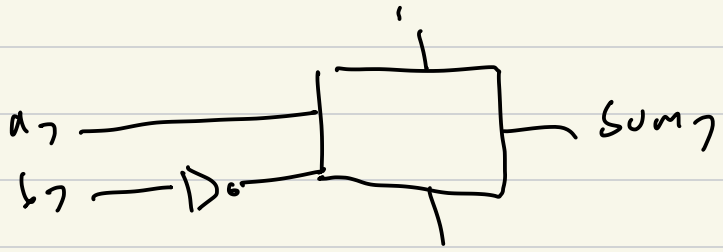

Combinational Logic

↳ components
Multiplexer
Decoder

Sequential Logic

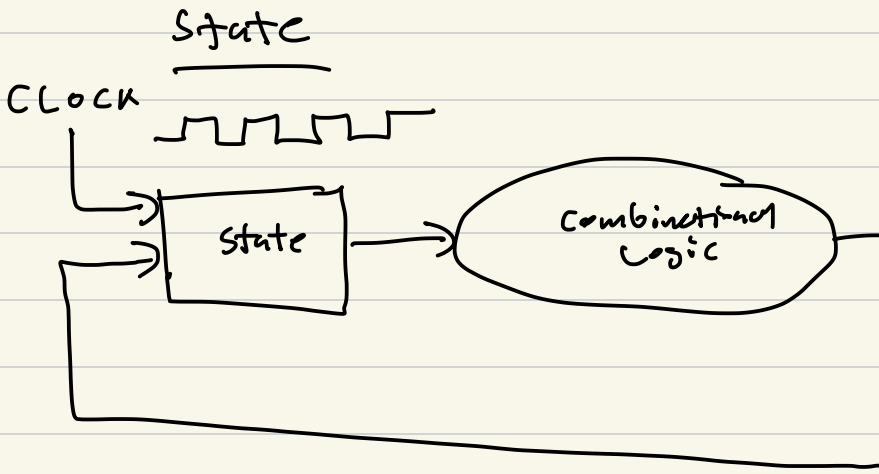

processor