
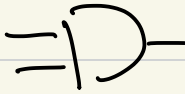


CS315-02 Combinational Logic Adder


AND

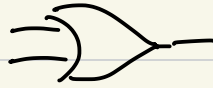


OR




NOT

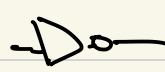

sum-of-products

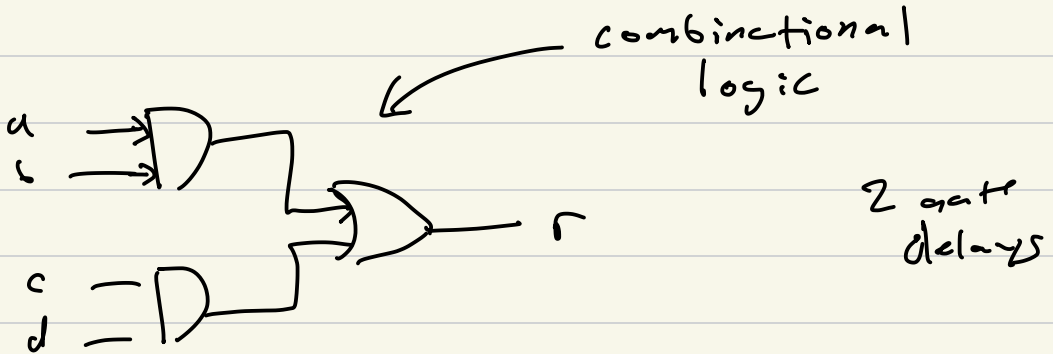

Goal:

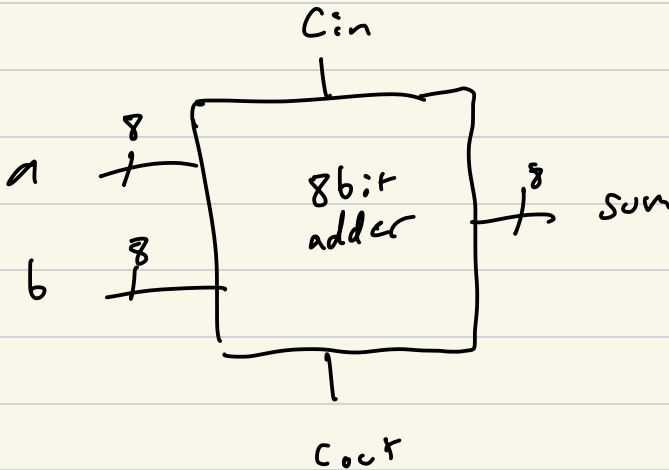

Sum-of-products

A new function

3-bit number $n_2 n_1 n_0$ (bits)

Two 1 bit outputs: even odd

Goal: determine if number of "1" bits is even or odd

1 1 0	even
1 0 1	even
1 0 0	odd
1 1 1	odd


sum-of-product

- 1) truth table
- 2) identify rows with output of 1
- 3) form SOP equation

	n_2	n_1	n_0	even	odd
①	0	0	0	1	0
	0	0	1	0	1
	0	1	0	0	1
②	0	1	1	1	0
	1	0	0	0	1
③	1	0	1	1	0
④	1	1	0	1	0
	1	1	1	0	1

$$\text{even} = (\bar{n}_2 \cdot \bar{n}_1 \cdot \bar{n}_0) + (\bar{n}_2 \cdot n_1 \cdot n_0) + (n_2 \cdot \bar{n}_1 \cdot n_0) + (n_2 \cdot n_1 \cdot \bar{n}_0)$$

$$\text{odd} = \overline{\text{even}}$$

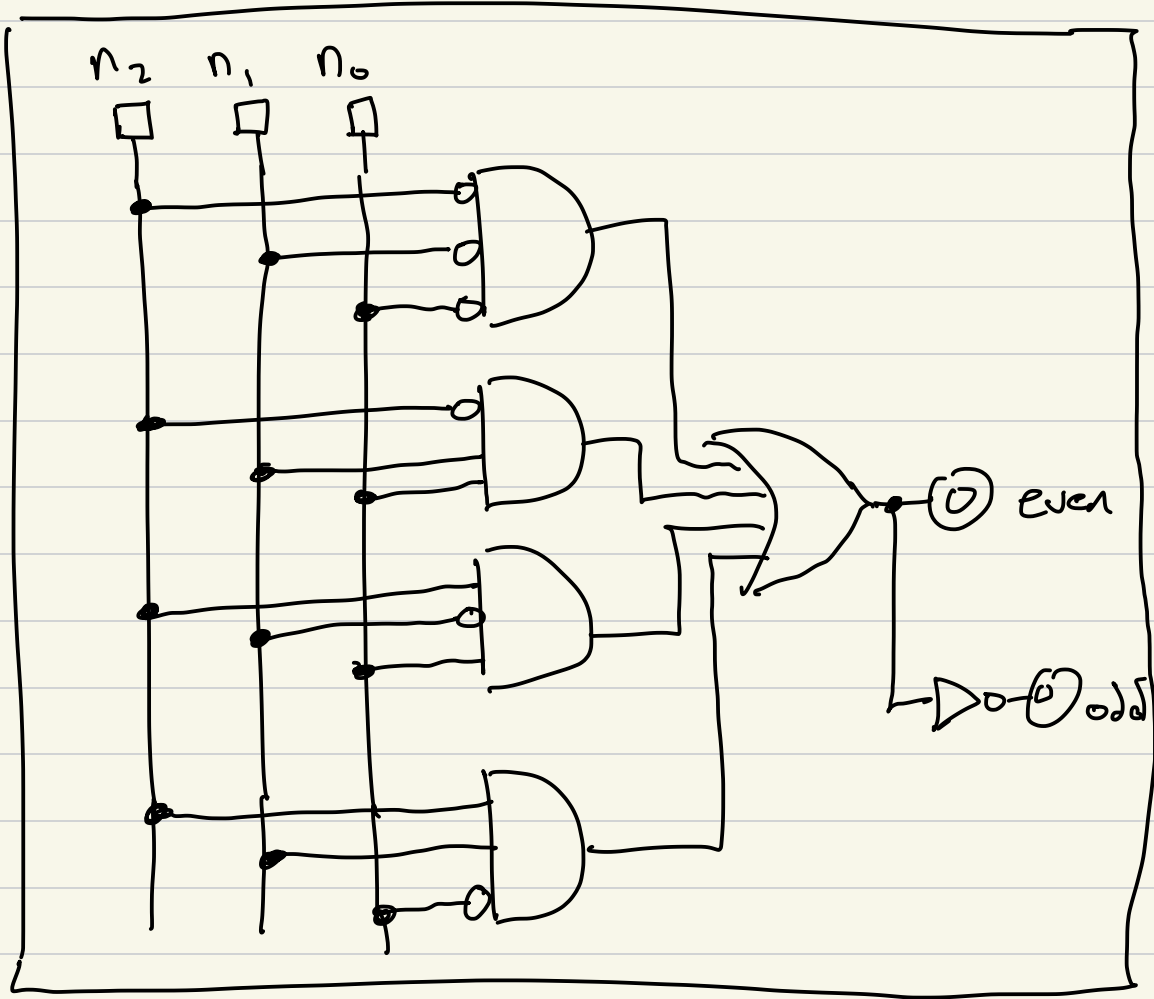

Digital Components

even-odd-bits

even-odd-multi:

Lab 04

Part 2

Max 2

2bit

$a_1 a_0$



2bit

$b_1 b_0$

2bit


$r_1 r_0$

max

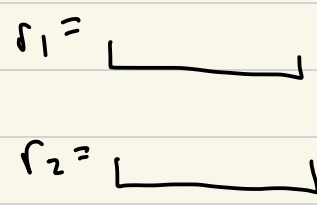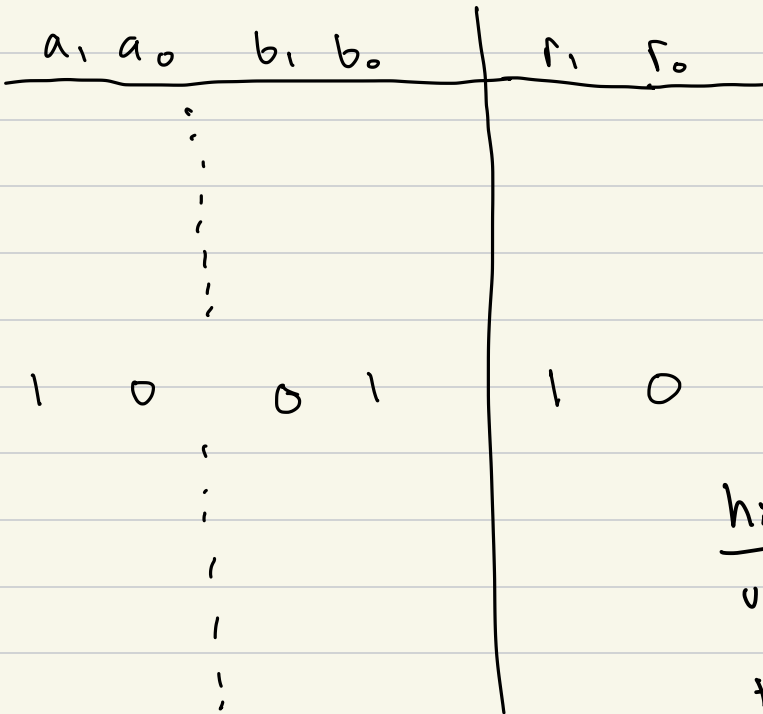


hint:
use not (invert)
to reduce the
number of
product terms

1 bit Adder

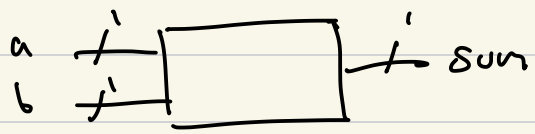


1 bit
half adder

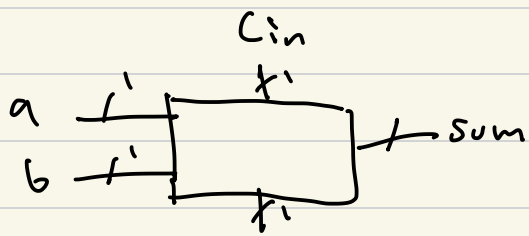


1 bit
full adder

Part 3
truth
table

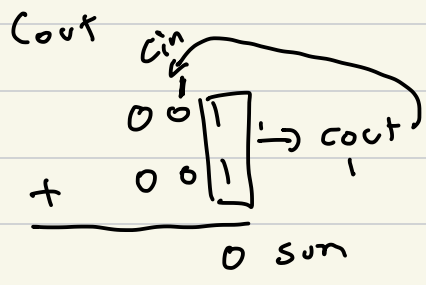


1 bit full adder

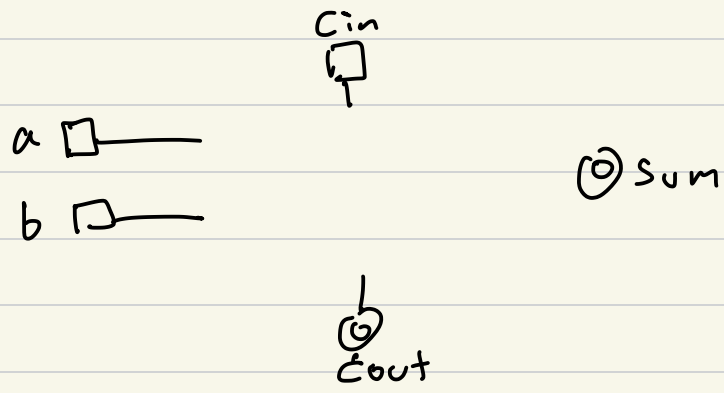


8 bit ripple carry adder
FA = full adder

$a_7 a_6 a_5 a_4 a_3 a_2 a_1 a_0$ $b_7 b_6 b_5 \dots$ c_{in}

How many
inputs:
17 bit
 2^{17}

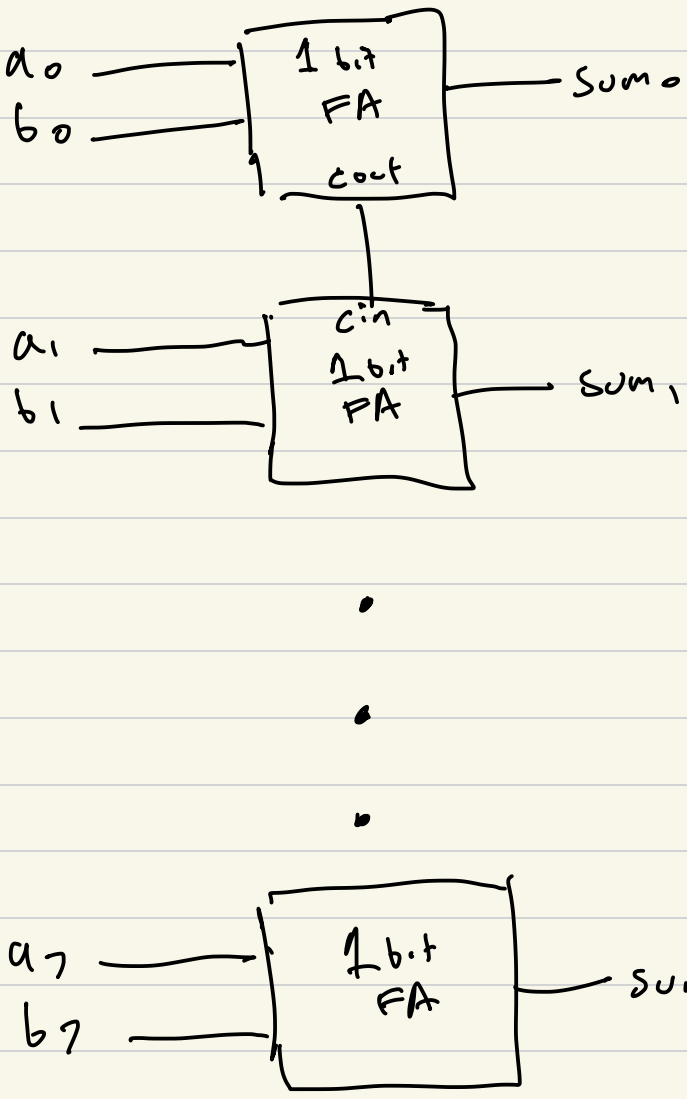

8 bit Ripple Carry Adder

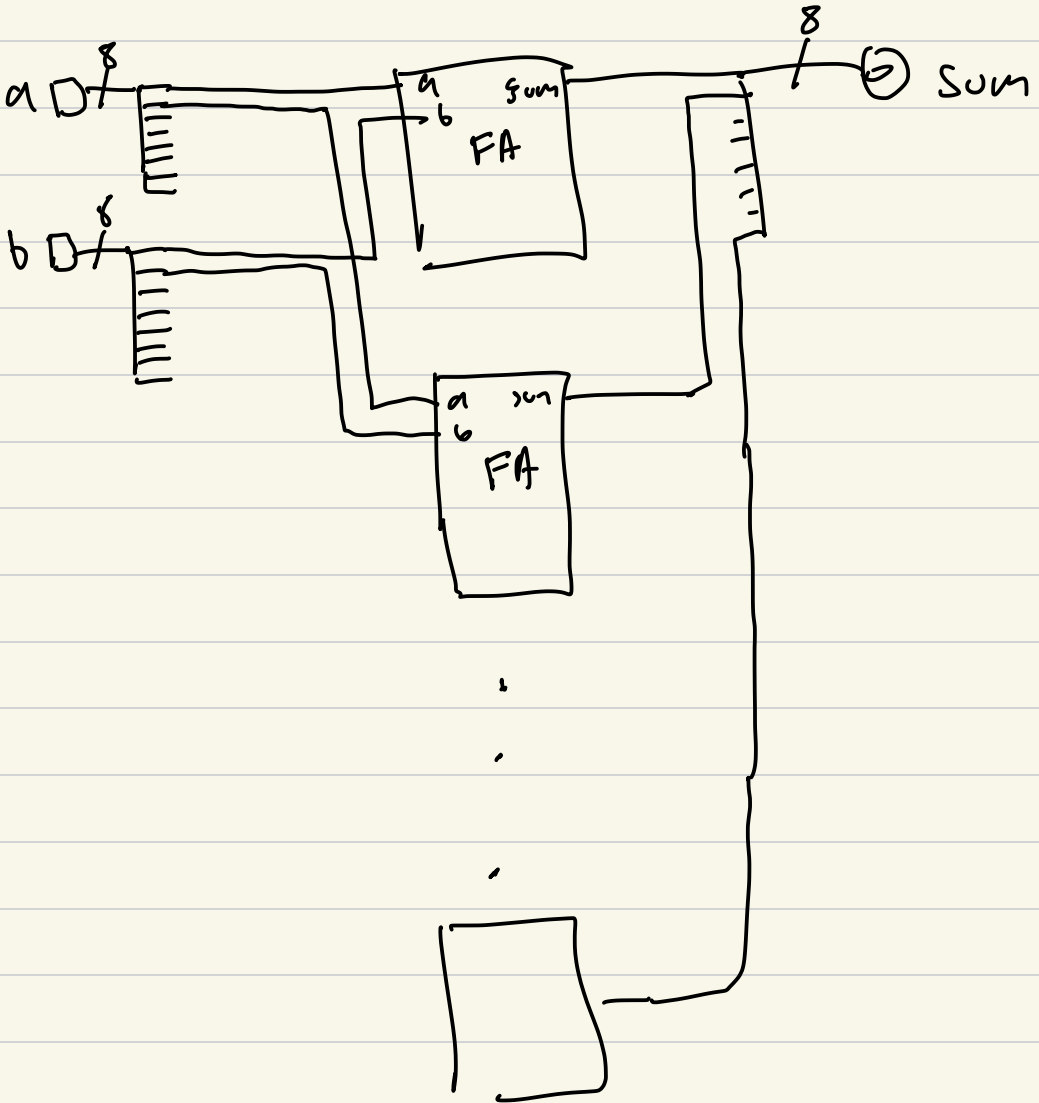


Subtraction



$$A - B == A + (-B)$$

invert
add 1

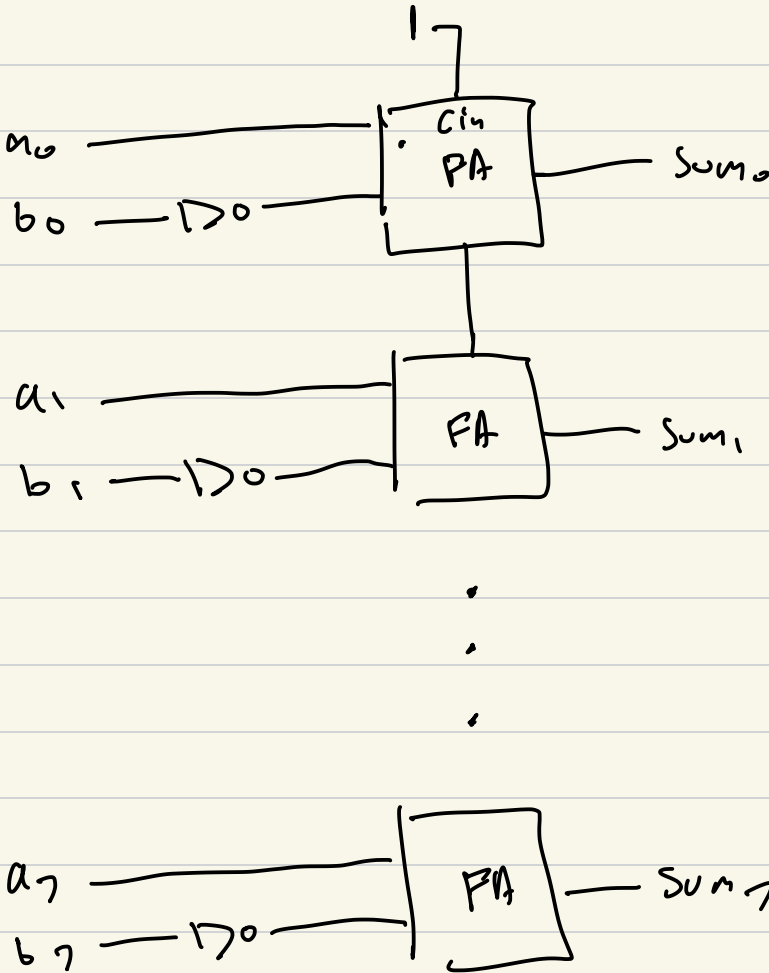

Combinational Logic

components

multiplexer
decoder

Sequential Logic

