
 


# CS 315-02 Processor Design Decoding

## Lab 05 - RegFile and ALU

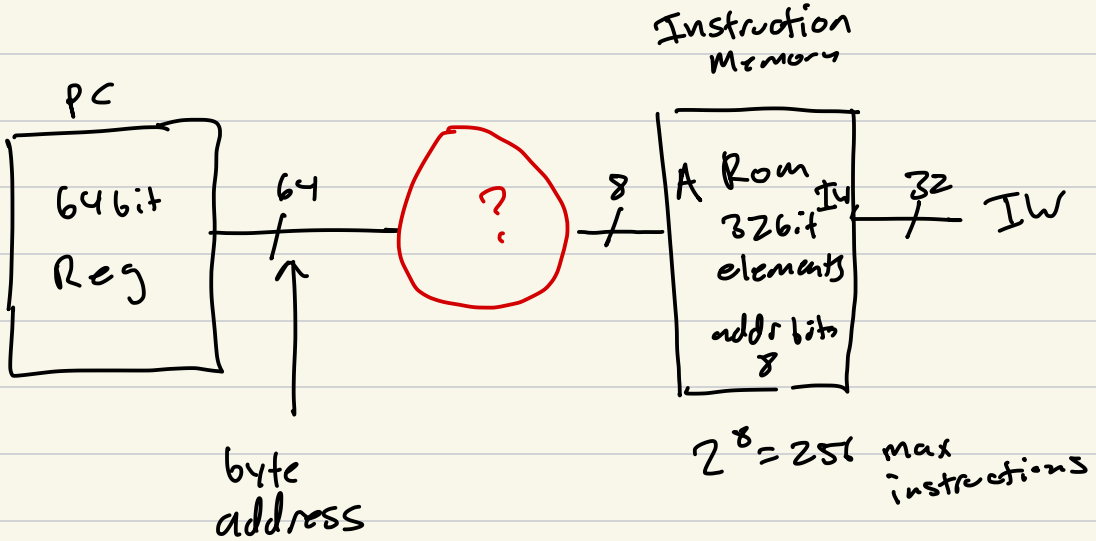


# Memory


addr\_byte

$$\text{addr\_word} = \text{addr\_byte} / 4$$

 
$$\text{addr\_word} = \text{addr\_byte} \gg 2$$



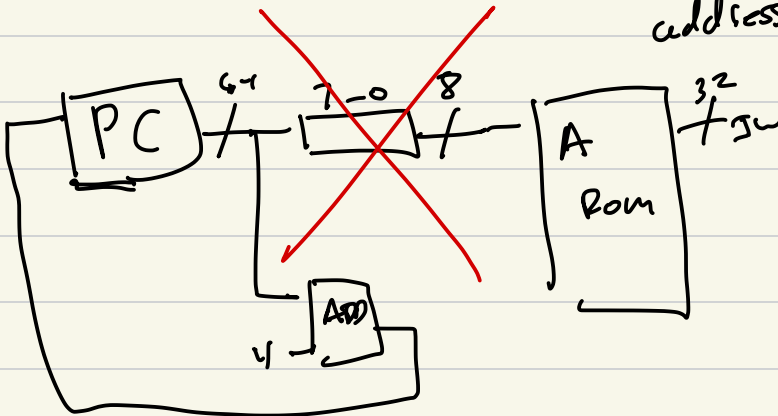
byte addresses  
word addresses  
8 bit byte



①


 



②

 

\*

③

  

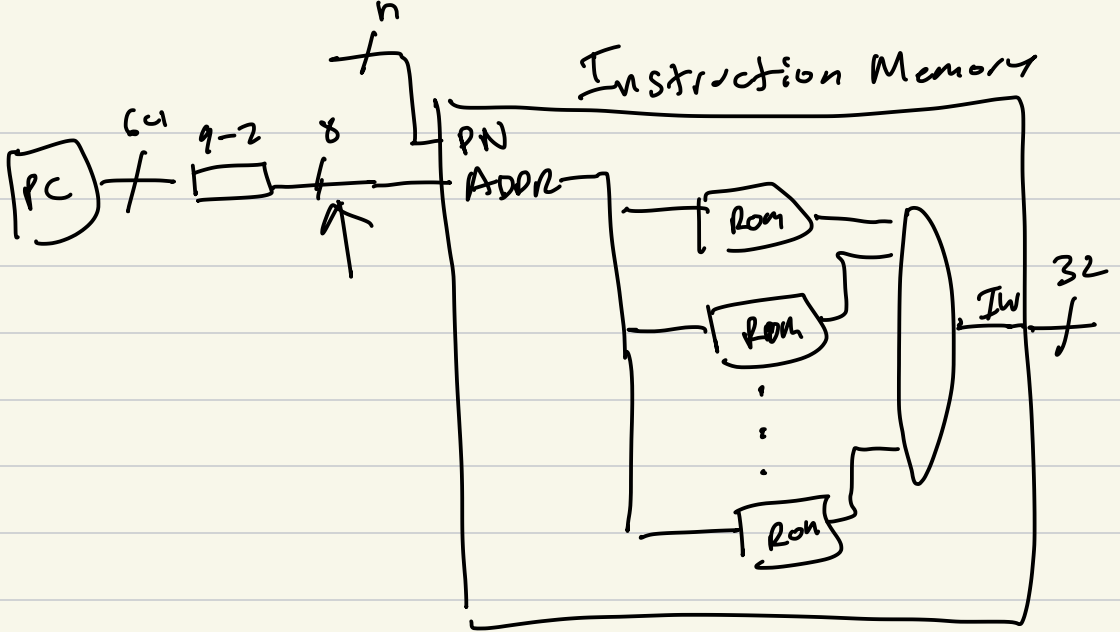


Decoding

Reg Decoder → get reg #s


Imm Decoder → form a 64 bit signed immediate

Inst Decoder →

 


Control lines


# Reg Decoder

 

⇒ Reg File


 


## One splitter

 


Can  
change  
order  
of splitter  
output


# Imm Decoder

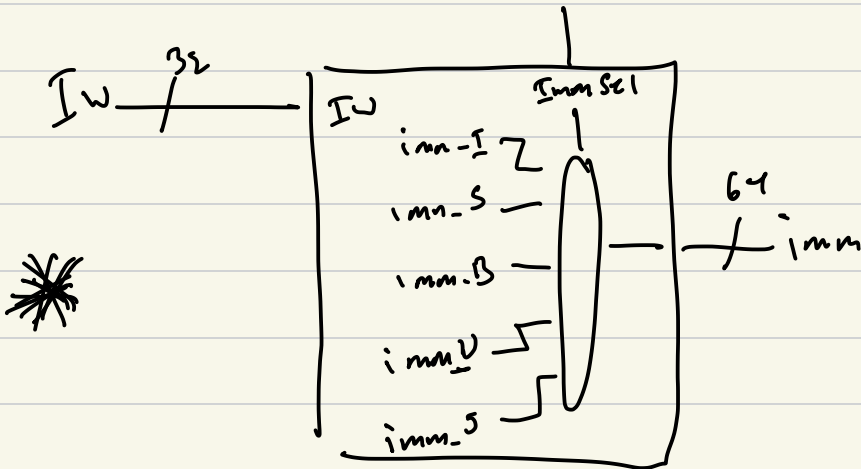 


# S-Type Immediate

 


Goal: To construct a 64-bit signed value

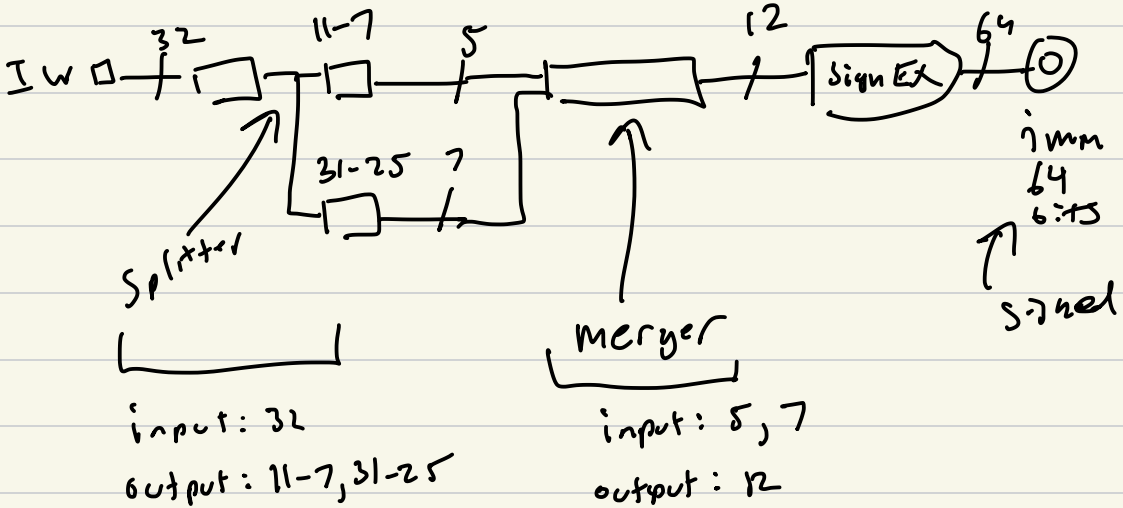

# How to implement the sign extender

 

## Option #1

 



Option #2

