

CS315-02 Processor Design Instruction Decoding

RegDecoder \rightarrow rs1, rs2, rd

ImmDecoder \rightarrow all immediates

64 bit two's comp signal value

Instruction Decoding (Inst Decoder)

IW \rightarrow control lines (signals)

To add new instructions

1) Add or modify components



2) Add more datapath wires/buses

3) Often this will require new or modified MUXes


4) Update Inst Decoder

possibly add new control lines


Inst Decoder

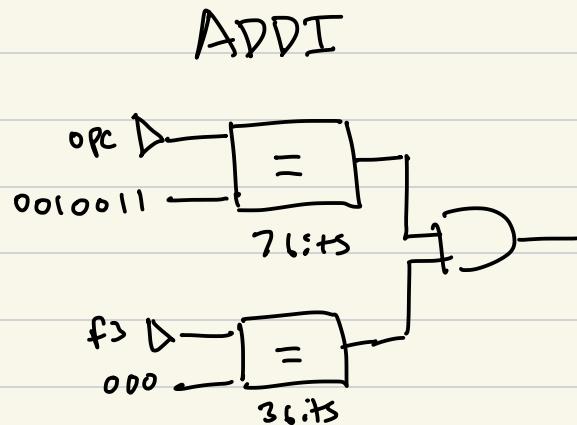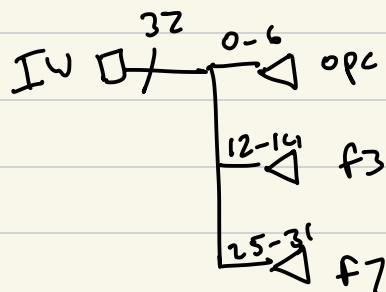


ADD

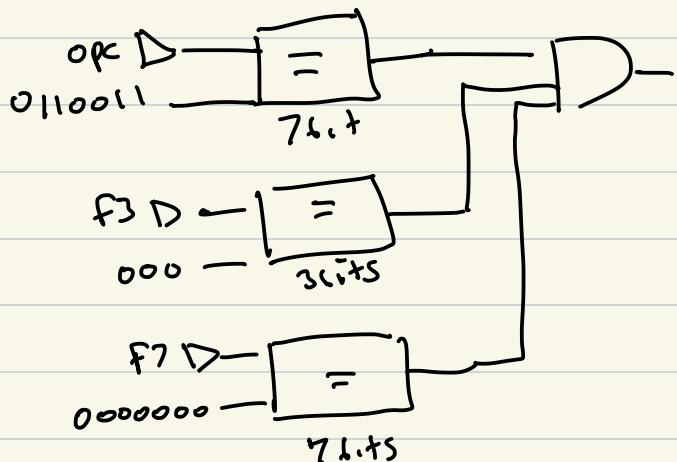


- ① ALU&SF
- ② ALU&OP
- ③ ALU&FW

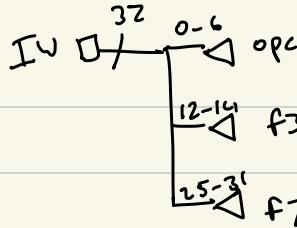


ADDI

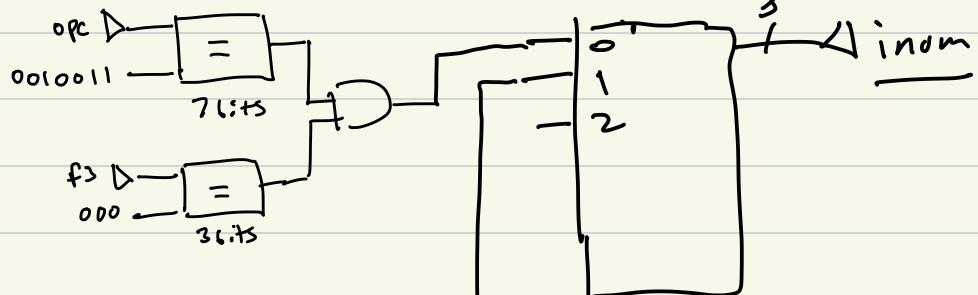

ADD

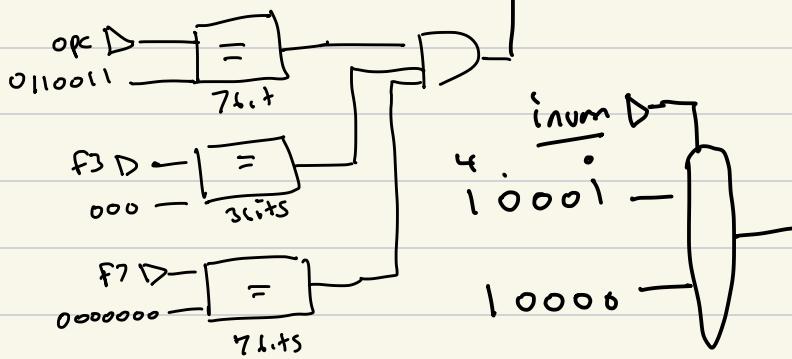

inst	RFW	ALUop	ALUSrcB
addi	1	000	1]
add	1	000	0]

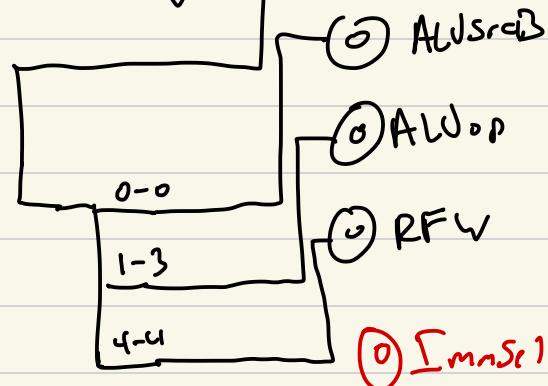

④ ImmSrc

